

11. Electricity and Magnetism (Spring 2003)

Secret Circuit: A two-terminal "black box" is given to you. Inside the box a circuit is attached to the terminals which is known to contain a lossless inductor L , a lossless capacitor C , and a resistor R . When a 1.5 Volt battery is connected across the terminals, a current of 1.5 milliamperes flows. When an AC voltage of 1.0 Volt (RMS) at a frequency of 60 Hz is connected, a current of 0.01 amperes (RMS) flows. As the AC frequency is increased while the applied voltage is maintained constant, the current is found to go through a maximum exceeding 100 amperes at $\nu = 1000$ Hz. What is the circuit inside the box? What are the values of R , L , and C ?

The requirements on the circuit are

- Resistor of resistance $R = \frac{V}{I} = \frac{1.5V}{1.5mA} = 1000\Omega$ is in it
- Inductor L is not in parallel or it would short circuit
- Capacitor C is not in series or it would block DC.
- Inductor and Capacitor are in series so there is a resonant frequency at which the impedance goes to zero

So the possible circuits are



Now we solve for C and L by applying the conditions

$$Z(\omega = 2\pi \cdot 60 \text{ Hz}) = \frac{V}{I} = \frac{1.0V}{0.01A} = 100\Omega$$

$$Z(\omega = 2\pi \cdot 1000 \text{ Hz}) = \frac{V}{I} = \frac{1.0V}{100A} \approx 0$$

For the first circuit, $\frac{1}{Z} = \frac{1}{R} + \frac{1}{Z_L + Z_C} = \frac{1}{R} + \frac{1}{i\omega L + \frac{1}{i\omega C}} = \frac{1}{R} + \frac{i\omega C}{1 - \omega^2 LC}$

So there is a frequency of zero impedance at $\omega^2 = \frac{1}{LC} \Rightarrow \omega = \sqrt{\frac{1}{LC}}$

$$\Rightarrow LC = \frac{1}{\omega^2} = \frac{1}{4\pi^2 \cdot 10^6 \text{ Hz}^2}$$

Now using the first condition, $\frac{1}{100\Omega} = \left| \frac{1}{1000\Omega} + \frac{i(2\pi \cdot 60 \text{ Hz})C}{1 - (2\pi \cdot 60 \text{ Hz})^2 LC} \right|$

$$\Rightarrow \frac{1}{100\Omega} \approx \left| \frac{1}{1000\Omega} + i(2\pi \cdot 60 \text{ Hz})C \right|$$

$$\Rightarrow 10^{-4} \Omega^{-2} \approx 10^{-6} \Omega^{-2} + (2\pi \cdot 60 \text{ Hz})^2 C^2$$

$$\Rightarrow 10^{-4} \Omega^{-2} \approx (2\pi \cdot 60 \text{ Hz})^2 C^2$$

$$\Rightarrow 10^{-3} \Omega^{-1} \approx 2\pi \cdot 60 \text{ Hz} C$$

$$\Rightarrow C \approx \frac{1}{12\pi} \text{ mF}$$

$$\Rightarrow L = \frac{1}{4\pi^2 \cdot 10^6 \text{ Hz}^2} \frac{1}{C} = \frac{12\pi \cdot 10^3}{4\pi^2 \cdot 10^6} \text{ H} = \frac{3}{\pi} \text{ mH}$$